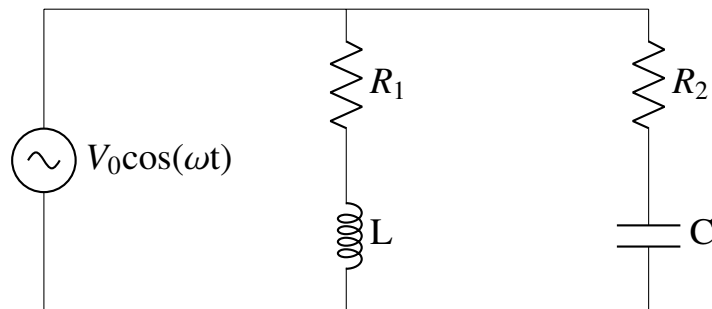


GATE 2023 Assignment

EE1205 Signals and Systems

Kurre Vinay
EE23BTECH11036

Question: In the circuit shown, $\omega = 100\pi \text{ rad/s}$, $R_1 = R_2 = 2.2\Omega$ and $L = 7 \text{ mH}$. the capacitance C for which Y_{in} is purely real is _____ mF



(GATE IN 2023)

Solution:

From *Table I*

| variable | value | description | formulae |
|------------|------------------------|---------------------------|---|
| Y_{in} | ?? | Admittance of circuit | $\frac{R_1 - Ls}{R_1^2 - (Ls)^2} + \frac{R_2 - \frac{1}{sC}}{R_2^2 - (\frac{1}{sC})^2}$ |
| X_L | $7s\Omega$ | Inductive reactance | sL |
| X_C | $\frac{1}{sC}\Omega$ | Capacitive reactance | $\frac{1}{sC}$ |
| s | $100\pi j$ | Laplace complex frequency | $j\omega$ |
| ω | $100\pi \text{ rad/s}$ | Angular frequency | - |
| V | $V_0 \cos(\omega t)$ | voltage of source | - |
| R_1, R_2 | 2.2Ω | resistance of resistors | - |

TABLE I

TABLE: INPUT PARAMETERS

$$Y_{in} = \frac{R_1 - Ls}{R_1^2 - (Ls)^2} + \frac{R_2 - \frac{1}{sC}}{R_2^2 - \left(\frac{1}{sC}\right)^2} \quad (1)$$

$$\text{Im}(Y_{in}) = \frac{-Ls}{R_1^2 - (Ls)^2} + \frac{-\frac{1}{sC}}{R_2^2 - \left(\frac{1}{sC}\right)^2} \quad (2)$$

According to the question given, Y_{in} is purely real, so imaginary part should be equal to zero

Take the values from *Table I*

$$\frac{-7(100\pi)}{(2.2)^2 + (7(100\pi))^2} + \frac{\frac{1}{(100\pi)C}}{(2.2)^2 + \left(\frac{1}{C(100\pi)}\right)^2} = 0 \quad (3)$$

$$\frac{-1}{4.4} + \frac{\frac{1}{(100\pi)C}}{(2.2)^2 + \left(\frac{1}{(100\pi)C}\right)^2} = 0 \quad (4)$$

$$\frac{\frac{1}{(100\pi)C}}{(2.2)^2 + \left(\frac{1}{(100\pi)C}\right)^2} = \frac{1}{4.4} \quad (5)$$

$$(2.2)^2 - \frac{4.4}{(100\pi)C} + \left(\frac{1}{(100\pi)C}\right)^2 = 0 \quad (6)$$

$$\left(2.2 - \frac{1}{(100\pi)C}\right)^2 = 0 \quad (7)$$

$$\frac{1}{(100\pi)C} = 2.2 \quad (8)$$

$$C = \frac{700}{484} \text{mF} \quad (9)$$

$$C = 1.446281 \text{mF} \quad (10)$$

The capacitance of capacitor C is 1.45mF

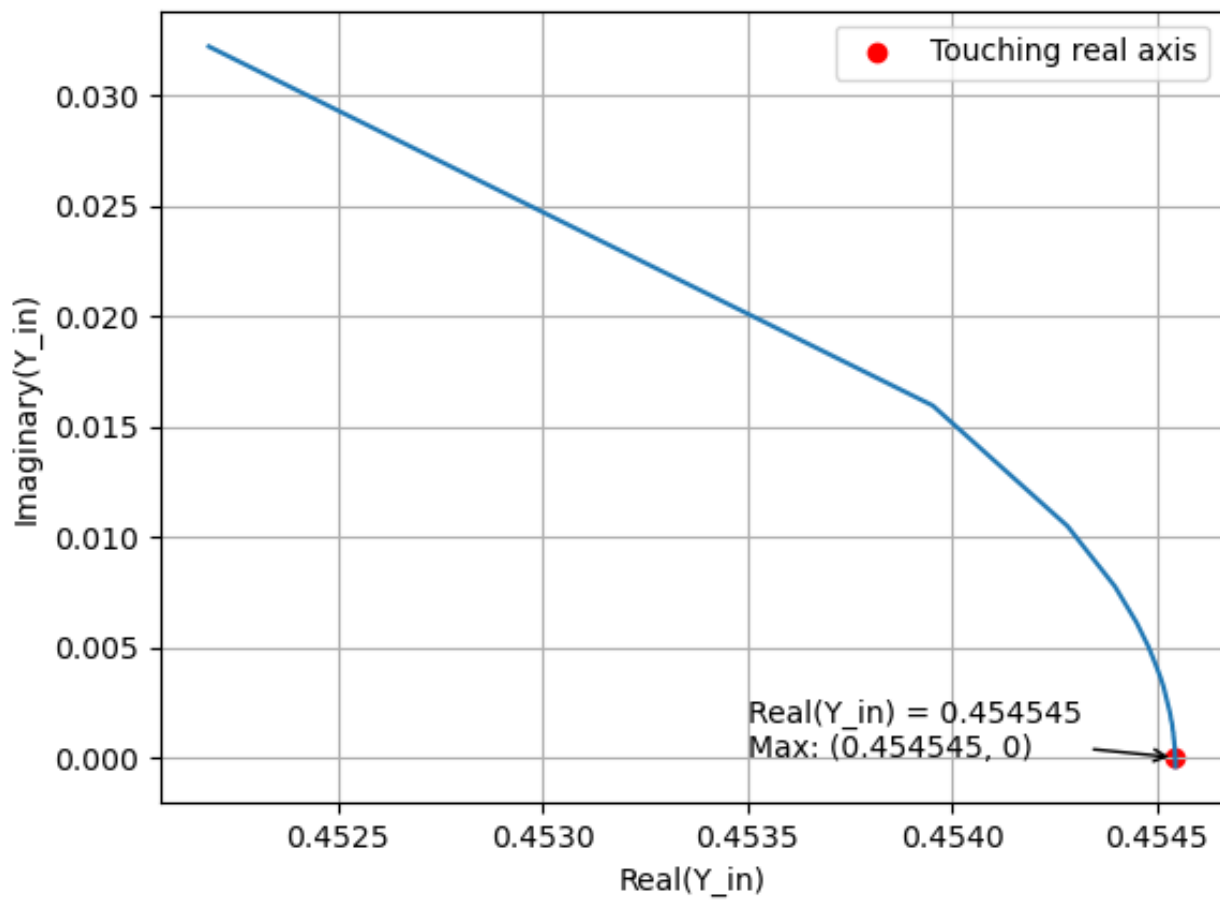


Fig. 1. the graph of admittance(Y_{in}) amplitude